

Total number of printed pages-4

44 (Sem-2) DLF (HC-2026/2.3) N/O

2022

DIGITAL LOGIC FUNDAMENTALS

Paper : BCA-HC-2026/BCA-2.3

Full Marks : 80

Time : Three hours

The figures in the margin indicate full marks for the questions.

1. Fill in the following blanks with appropriate words : $1 \times 10 = 10$

(i) For a 2 input logic gate the output will be 1 when both the inputs are 1 is _____ gate.

(ii) The SOP in Boolean logic stands for _____.

(iii) The _____ gate is known as a universal logic gate.

(iv) The binary equivalent of decimal 10 is _____.

(v) If A and B is a Boolean variable then the expression $A * B$ can be realized with _____ logic gate.

Contd.

- (vi) A full adder consists of _____ number of inputs and _____ number of outputs.
- (vii) A 4:1 multiplexer has 4 inputs data line and _____ input of select lines.
- (viii) A R-S flip flop can be considered as _____ circuit.
- (ix) A 3-bit ripple counter will have _____ number of logic states.
- (x) The storage of 1 KB of memory consists of _____ number of bites.

2. Very short answer type questions : $2 \times 5 = 10$

- (a) Convert the following
 - (i) (1010.1010) binary to decimal,
 - (ii) (27) decimal to binary
- (b) Write the truth table for a 2-input NAND gate.
- (c) What is the difference between a latch and a flip-flop ?
- (d) Distinguish combinational and sequential logic circuits.
- (e) Write down the truth table for a half-subtractor.

3. Short from answer type question : (answer **any four** questions from the following)

$5 \times 4 = 20$

- (i) Write down the two De-Morgan's theorem of Boolean algebra. State and prove the two theorems with appropriate logic circuits.

- (ii) What is a full adder logic circuit? Write the truth table of full adder and design the full adder with appropriate logic diagram.
- (iii) What is a flip-flop? How is it different from a latch? Discuss the working of R-S flip flop with appropriate timing diagram.
- (iv) What is a shift register? What are the different types of shift registers used in digital system design? Explain briefly.
- (v) What is a don't care variable in a Karnaugh map simplification method? Discuss the role of a don't care in a 3-variable k-map method.
- (vi) Why NAND and NOR gate is called universal logic gates? Design two input AND, OR and NOT operation using 2-input NAND gate only.

4. Answer **any four** from the following :

10×4=40

(a) Write a short note on the different postulates and basic theorems of Boolean algebra.

(b) Simplify the following SOP terms using k-map simplification method.

(i) $f(A, B, C) = \sum(0, 2, 4, 5, 7)$

(ii) $f(A, B, C, D) = \sum(1, 4, 5, 7, 10, 11, 12)$

(c) What is a combinational logic circuit? What are the different combinational logic circuits, write a short note on it? Simplify the following Boolean expression. $F = (\bar{A} + B)(A + \bar{C})(\bar{B} + \bar{C})$

(d) What is a sequential logic circuit? What is J-K flip flop? Write the truth table of a J-K flip flop and discuss its operation.

(e) What is binary counter? What is the difference between asynchronous counter and synchronous counter? Design a 3-bit ripple counter with its circuit diagram.

(f) Write a short note on *any two* of the following :

(i) Serial-in, serial-out shift register

(ii) Parallel-in parallel-out shift register

(iii) 3-to-8-line decoder

(iv) 4:1 multiplexer

